

logic gates


→ logic gates are the basic building blocks of any digital system.

→ It is an electronic circuit having one or more input and only one output.

→ The relationship between the input and the output is based on a certain logic.

How do logic gates work??

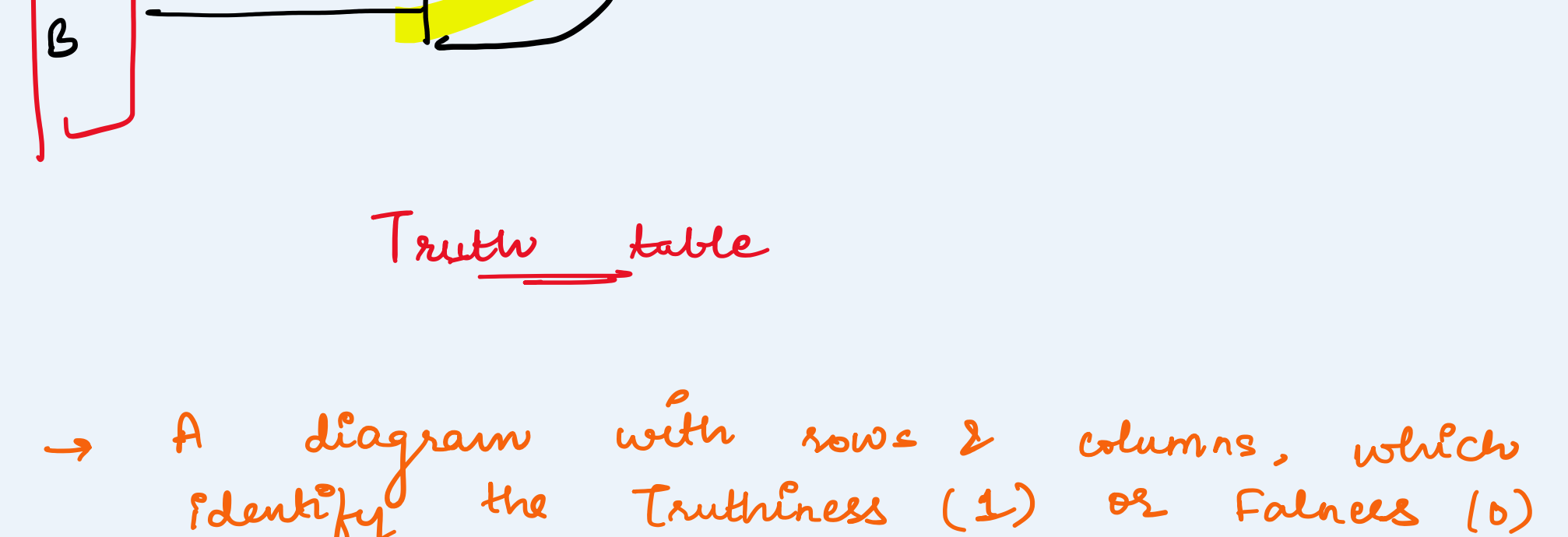→ logic gates will take input in the form of binary digits (0 or 1) and output a single binary digit representing a boolean function




Truth table

→ A diagram with rows & columns, which identify the Truthiness (1) or Falseness (0) of a compound statement, or in this case logic gates circuit.

AND Gate

Output → 1 if both the input pins provide 1 input as

logic diagram

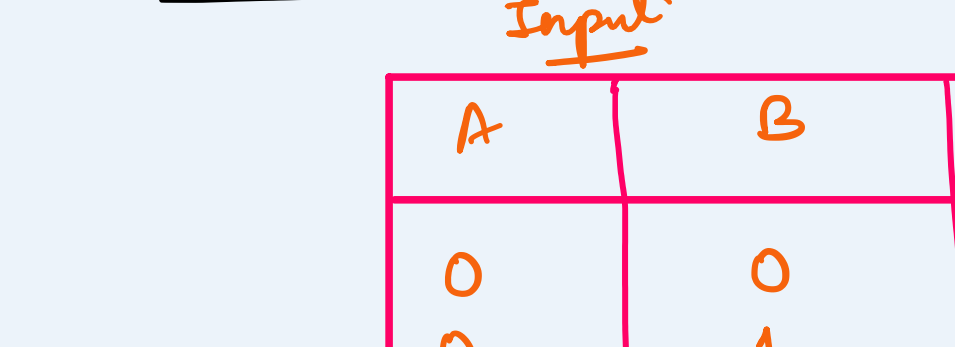


Truth table

Input		Output
A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate

Output → 1 if any of the input pins has 1.

logic diagram

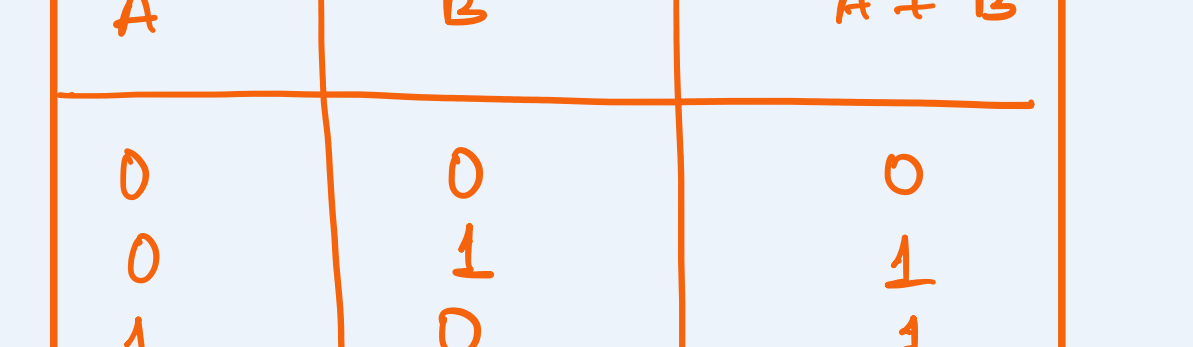


Truth table

Input		Output
A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

NOT gate

1 → 0
0 → 1

logic diagram

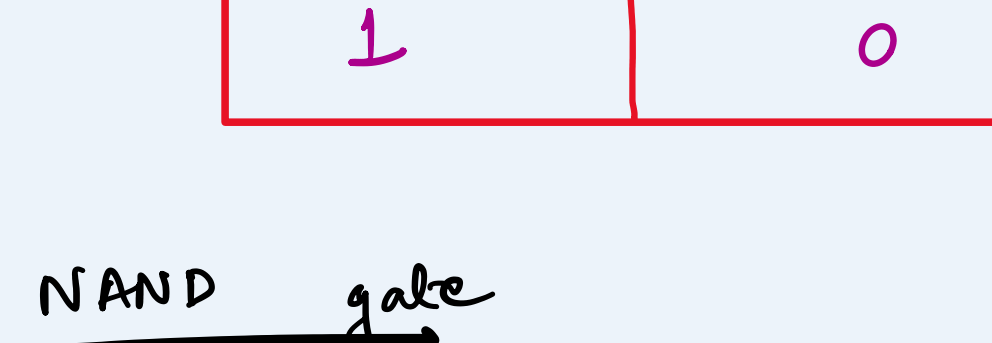


Truth table

Input	Output
A	Y
0	1
1	0

NAND gate

NOT - AND gate

logic diagram

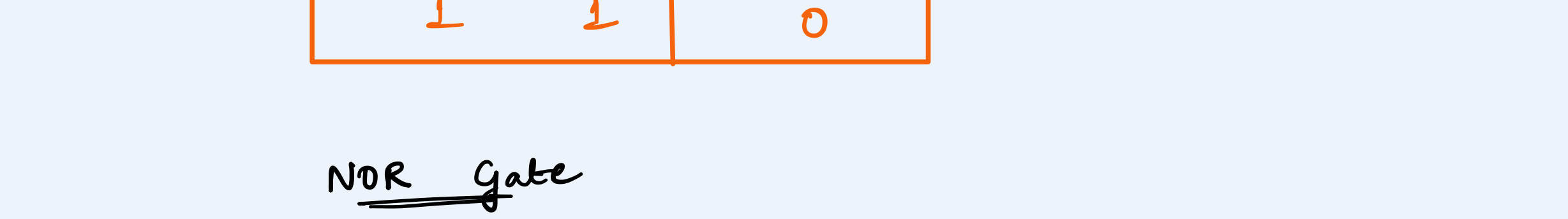


Truth table

Input		Output
A	B	$\overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR gate

NOT - OR gate

logic diagram

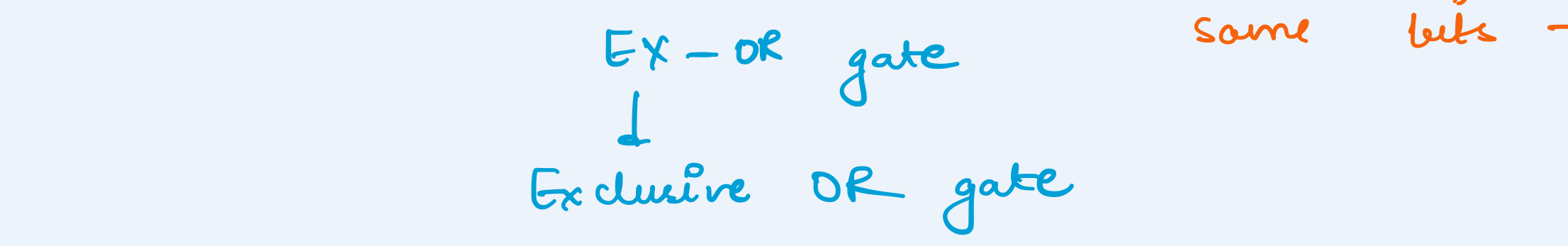


A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

XOR gate

Ex-OR gate
Exclusive OR gate

different bits → 1
same bits → 0

logic diagram

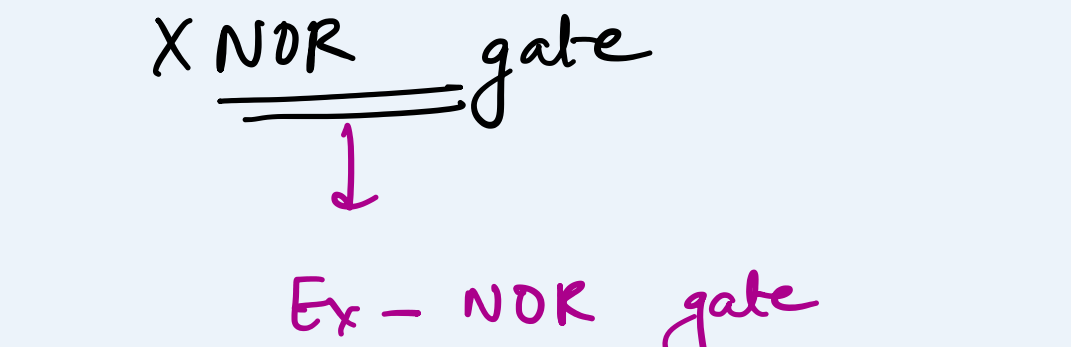


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


XNOR gate

Ex-NOR gate
Exclusive NOR gate

logic diagram

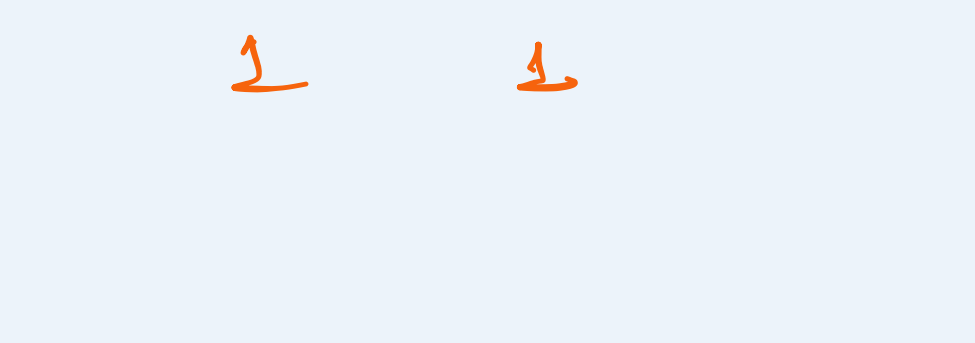

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

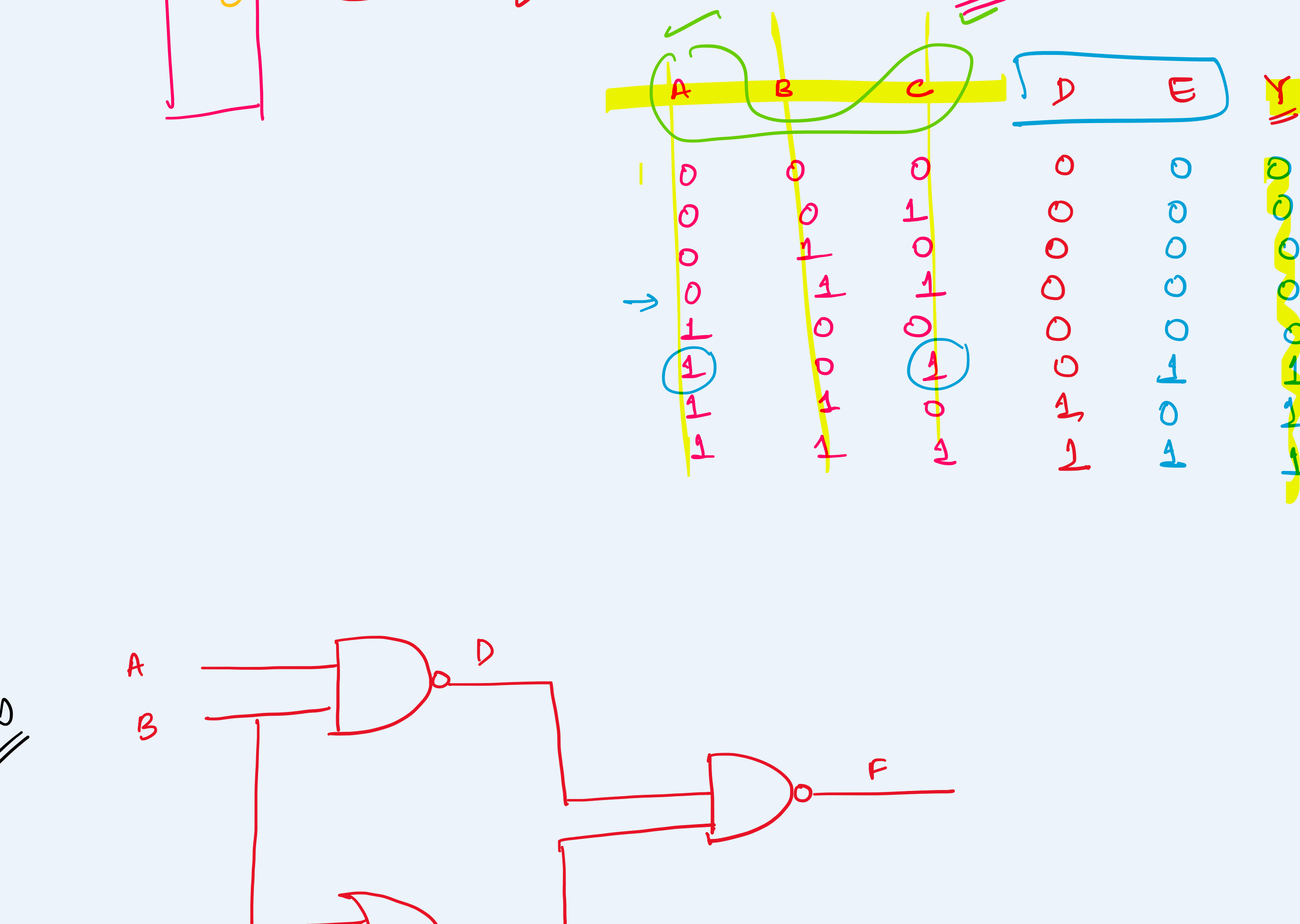

logic gates with 2 input pins

